Visit **www.brpaper.com** for downloading previous years question papers of
10th and 12th (PSEB and CBSE), IKPTU,MRSSTU, PSBTE, PANJAB UNIVERSITY,
PUNJABI UNIVERSITY, BFUHS, HPTU, HPSBTE , HARYANA DIPLOMA, MDU HARYANA

Roll No. | | | | | | | | | | | | | **Total No. of Pages : 02**

Total No. of Questions : 18

B.Tech. (Electrical & Electronics) (2018 Batch) (Sem.–4)

DIGITAL ELECTRONICS

Subject Code : BTEE-401-18

M.Code : 77606

Time : 3 Hrs. **Max. Marks : 60**

INSTRUCTIONS TO CANDIDATES :

1. **SECTION-A is COMPULSORY consisting of TEN questions carrying TWO marks each.**
2. **SECTION-B contains FIVE questions carrying FIVE marks each and students have to attempt any FOUR questions.**
3. **SECTION-C contains THREE questions carrying TEN marks each and students have to attempt any TWO questions.**

SECTION-A

Write briefly :

Q1. Define Noise Margin?

Q2. State the different classification of binary codes.

Q3. State the commutative property of Boolean algebra.

Q4. What is Propagation Delay?

Q5. What is a Karnaugh Map?

Q6. Give the comparison between synchronous & Asynchronous sequential circuits.

Q7. State and prove De Morgan's theorem.

Q8. Obtain the canonical sum of products of the function Y = AB + ACD.

Q9. What is EEPROM?

Q10. Which gates are called as the Universal Gates? What are its advantages?

brpaper.com
brpaper.com

BR paper
exams preparatory

SECTION-B

Q11. Simplify the given expression AB + (AC)' + AB'C (AB + C).

Q12. Explain the flip-flop excitation tables for JK flip-flop.

Q13. State the postulates and theorems of Boolean algebra.

Q14. Design and explain a comparator to compare two identical words.

Q15. Explain in detail about Race around condition.

SECTION-C

Q16. Determine the prime implicants of the function

F (W,X,Y,Z) = _ (1,4,6,7,8,9,10,11,15)

Q17. Explain with neat diagrams TTL.

Q18. Explain the working of BCD Ripple Counter with the help of state diagram and logic Diagram.

brpaper.com

brpaper.com

NOTE : Disclosure of Identity by writing Mobile No. or Making of passing request on any page of Answer Sheet will lead to UMC against the Student.